ⁱ FrontpageTFY4190

Department of Physics, NTNU

Examination paper for TFY4190 Instrumentation

Examination date: **June 10, 2021** Examination time (from-to): **9-13**

Permitted examination support material: A / All support material is allowed

Academic contact during examination: Steinar Raaen Phone: 48 29 67 58

Technical support during examination: Orakel support services Phone: 73 59 16 00

If you experience technical problems during the exam, contact Orakel support services as soon as possible <u>before the examination time expires</u>. If you don't get through immediately, hold the line until your call is answered.

OTHER INFORMATION

Make your own assumptions: If a question is unclear/vague, make your own assumptions and specify them in your answer. Only contact academic contact in case of errors or insufficiencies in the question set.

Saving: Answers written in Inspera Assessment are automatically saved every 15 seconds. If you are working in another program remember to save your answer regularly.

Cheating/Plagiarism: The exam is an individual, independent work. Examination aids are permitted, but make sure you follow any instructions regarding citations. During the exam it is not permitted to communicate with others about the exam questions, or distribute drafts for solutions. Such communication is regarded as cheating. All submitted answers will be subject to plagiarism control. <u>Read more about cheating and</u> <u>plagiarism here.</u>

Notifications: If there is a need to send a message to the candidates during the exam (e.g. if there is an error in the question set), this will be done by sending a notification in Inspera. A dialogue box will appear. You can re-read the notification by clicking the bell icon in the top right-hand corner of the screen. All candidates will also receive an SMS to ensure that nobody misses out on important information. Please keep your phone available during the exam.

Your answer will be submitted automatically when the examination time expires and the test closes, if you have answered at least one question. This will happen even if you do not click "Submit and return to dashboard" on the last page of the question set. You can reopen and edit your answer as long as the test is open. If no questions are answered by the time the examination time expires, your answer will not be submitted.

Withdrawing from the exam: If you become ill, or wish to submit a blank test/withdraw from the exam for another reason, go to the menu in the top right-hand corner and click "Submit blank". This cannot be undone, even if the test is still open.

Accessing your answer post-submission: You will find your answer in Archive when the examination time has expired.

¹ p1v2TFY4190v2021

The 2 complement representation of the decimal number -213 is: **Select one alternative:**

• 1010111

• 1101011


• 11010101

• 100101011

• 110101

(2 points for correct answer)

² p2v2TFY4190v2021

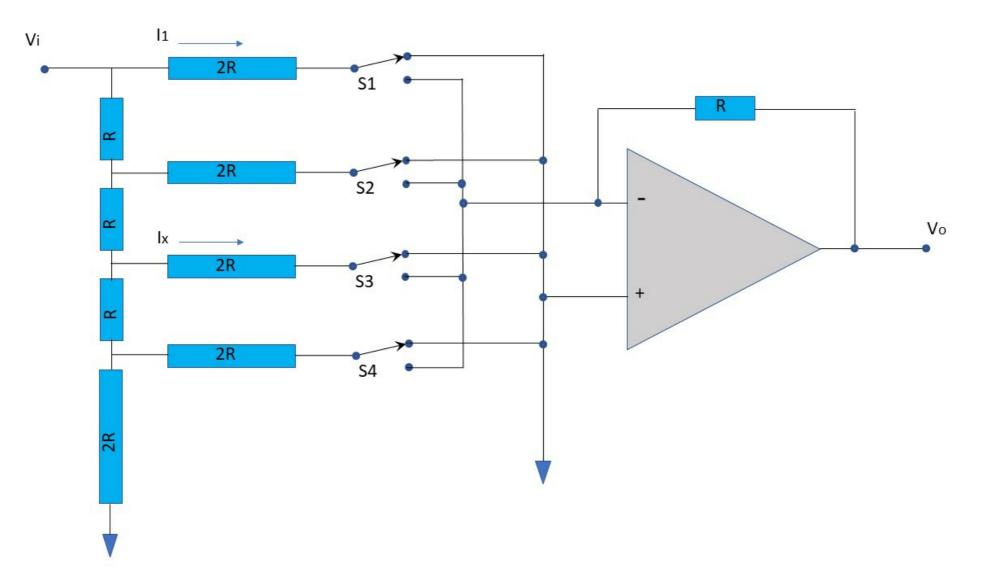

The DAC circuit shown above consists of resistors with resistances R and 2R as indicated, switches S1 to S4, and an ideal operational amplifier. The reference voltage is V_i and the output voltage is V_o . Currents I_1 and I_x are indicated in the figure.

What is the ratio I_1/I_x between currents I_1 and I_x ?

Enter the answer here:



What is the analogue output if switches S1, S2, and S3 are in the lower positions, and switch S4 is in the upper position? Assume a reference voltage V_i of 5 V.

Enter the answer here:



(2 points for each correct answer)

p3v1TFY4190v2021

3

A single precision binary number consists of 32 bits. The MSB gives the sign, the next 8 bits the exponent, and the 23 remaining bits give the fraction. A bias of 127 is used for the exponent. What is the decimal value of the single precision number given in hexadecimal form by C2380000?

Enter the answer here:

(2 points for correct answer)

⁴ p4v2TFY4190v2021

A physical quantity is measured 10 times. The results are: 5.1, 5.2, 5.0, 5.3, 4.9, 5.1, 5.2, 5,0, 4.8, 5.0 (in arbitrary units). What is the precision in % for the second measurement (value 5.2)? **Select one alternative:**

• 98	%		
9 7	%		
• 96	%		
• 95	%		
9 9	%		

(2 points for correct answer)

5 p5v2TFY4190v2021

Assume the following time dependent signal $y(t)=sin(\omega t)$.

Find the RMS (root mean square) average of the signal. The RMS average is:


0.67 0.83 0.71 0.5

0.64

Find the rectified average of the signal. The rectified average is:

0.67		
0.71		
0.64		
0.83		
0.5		

6 p6v3TFY4190v2021

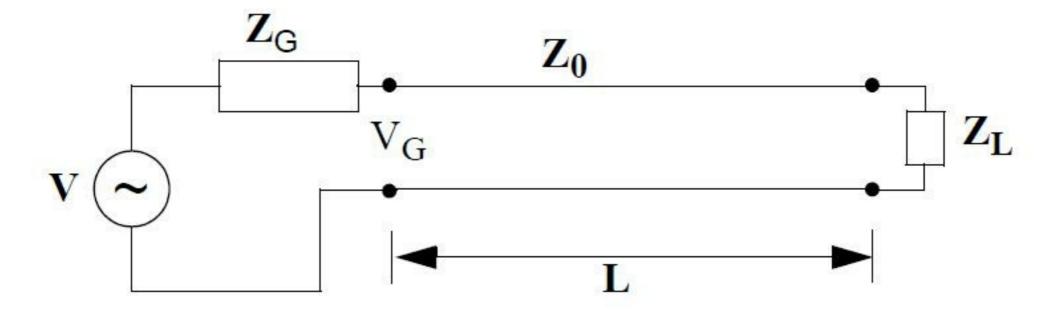

The figure above shows a generator circuit that transmit a high frequency signal on a transmission line of characteristic impedance Z_0 . At the end of the line is a load impedance $Z_L = 1000\Omega - i300\Omega$.

Which statement is correct? Select one alternative:

- the voltage signal is a maximum at the load
- the voltage increases when moving away from the load
- the voltage decreases when moving away from the load
- the voltage signal is a minimum at the load

The voltage standing wave ratio (VSWR) at the load is given by VSWR = 4. What is the magnitude of the reflection coefficient at the load? Select one alternative

0.4

0.5


0.6

• 0.7

0.8

(2 points for each correct answer)

⁷ p7v2TFY4190v2021

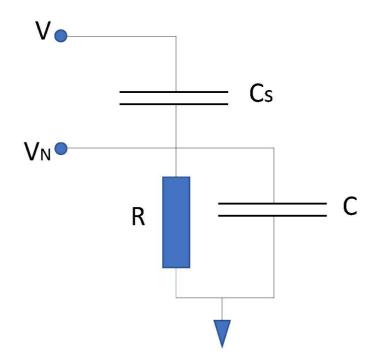

The input circuit of an amplifier can be considered to consist of a $R = 10M\Omega$ resistor in parallel with a C = 100pF capacitor as shown in the figure above. A power line of frequency f = 50Hz and peak to peak voltage V = 320V results in a noise voltage of $V_N = 1V$ at the input of the amplifier due to capacitive coupling.

Find the capacitance C_S between the power line and the input circuit. Select one alternative:

0.62 pF

1.04 pF

0.89 pF

0.52 pF

1.24 pF

8

(4 points for correct answer)

p8v2TFY4190v2021

A 16 bit ADC has operating range from -15 to +15V. The output signal is given in 2 complement binary format in hexadecimal representation V_{out} = 9DE3.

What is the resolution of the ADC?

Enter the answer here:

What is the input voltage?

Enter the answer here:

: V.

mV.

(2 points for each correct answer)

9 p9v2TFY4190v2021

Convert decimal 4038.356 to hexadecimal format. The answer is given by: Select one alternative:

- FC6.5B22...
- FC6.6011...

FC6.5B30...

FC6.5C1E...

FC6.4FF3...

(2 points for correct answer)

Maximum marks: 2

10 p10v1TFY4190v2021

A sound signal has bandwidth from 10 to 24000Hz. Only frequencies up to 18000Hz are of interest for a particular application. Assume that a digital sampling is to be done of the signal. What should the minimum sampling frequency be to avoid aliasing?

Select one alternative

- 36000 Hz
- 24000 Hz
- 18000 Hz

48000 Hz

What should the cut-off frequency be for the low-pass filter? Select one alternative

24000 Hz

18000 Hz

48000 Hz

36000 Hz

(1 point for each correct answer)

¹¹ p11v1TFY4190v2021



A disturbance in form of a sharp voltage pulse (delta pulse) is impinging on a system of transfer function F(s) as shown above. The transfer function of the measurement system is given by: $F(s) = \frac{s}{(s+1)(s+2)}$.


How large is the effect of the disturbance on the output signal y(t) after t = 0.5s?

Enter the answer in % of the maximum disturbance: %.

(4 points for correct answer)

Maximum marks: 4

¹² p12v1TFY4190v2021

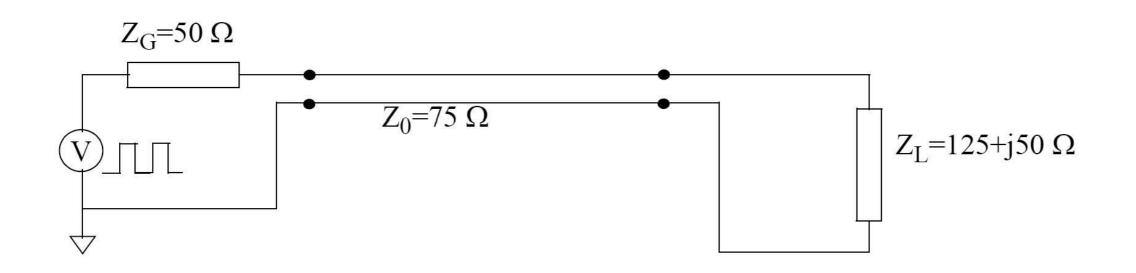


A high frequency pulse train enters a transmission line as shown in the figure. At the end of the transmission line is a complex load that consists of a serial coupling of a resistor and a solenoid. Find the reflection coefficients at the load. Give the answer in amplitude and phase angle. Assume loss-less transmission line.

The amplitude of the reflection coefficient is:	
The phase of the reflection coefficient is:	^o (degrees).

(2 points for each correct answer)

¹³ p13v1TFY4190v2021

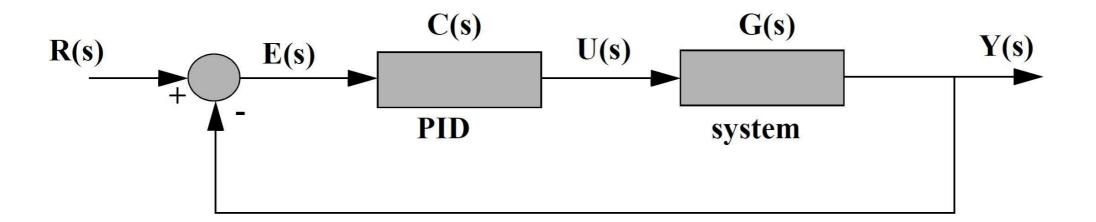

A PID regulated system is shown in the figure above.

The transfer function of the system is given by $G(s) = rac{1}{0.01s^3 + s + 1}$

rad/s.

Assume proportional control and harmonic signal and find the angular frequency where the regulated system starts to oscillate.

Enter the answer here:

Find the period of the oscillations at this point.

Enter the oscillation period here: s.

(1 point for each correct answer)


Maximum marks: 2

¹⁴ p14v1TFY4190v2021

A harmonic signal $u(t) = 5cos\omega t [V]$ is to be sampled by using a 14 bit ADC. The frequency of the signal is given by f = 1kHz. The signal should not increase by more than 25% of the resolution between samplings. Find the maximum sampling time that may be used for digitizing the signal.


Enter the maximum sampling time here: ns.

15 p15v1TFY4190v2021

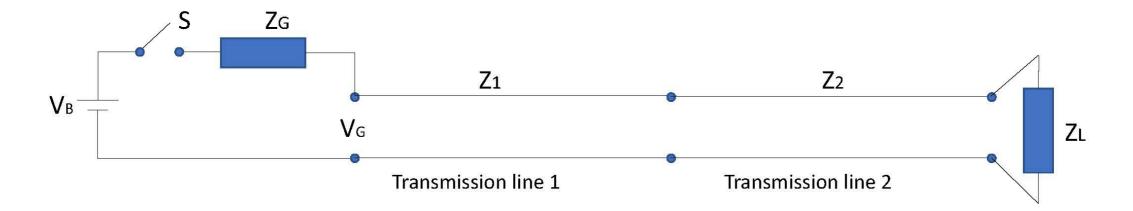

A battery of voltage V_B and a switch **S** generates a step voltage $V_G = 6V$ at the start of transmission line 1. Impedances are given by $Z_G = 75\Omega$ and $Z_1 = 75\Omega$. What is the voltage $\boldsymbol{V}_{\boldsymbol{B}}$ of the battery ?

Enter the voltage here: V.

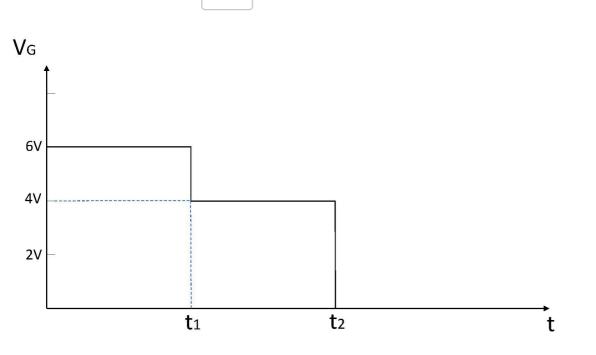

How V_G varies with time is shown in the figure above.

Find the line impedance of transmission line 2.

 Ω . Enter the line impedance **Z**₂ here:

Use the curve above to estimate the size of the load at the end of transmission line 2.

Enter the value of $\mathbf{Z}_{\mathbf{L}}$ here:

Ω.

(2 points for each correct answer)

¹⁶ p16v1TFY4190v2021

We want to sample the signal $u(t)=sin(\omega t)$. The angular frequency $\omega=56520~rad/s$. We will use sampling frequency $f_s=25~kHz$.

Which of the following frequencies may be reproduced in the sampled signal in the absence of a low-pass filter?

Select one or more alternatives:

- 18000 Hz
- 30000 Hz
- 40000 Hz
- 50000 Hz
- 20000 Hz
- 25000 Hz

(2 points for each correct answer, -2 points for each wrong answer, minimum score is 0 points)

Maximum marks: 6


¹⁷ p17v2TFY4190v2021

Consider a semiconductor junction of resistance $R = 100k\Omega$ which is at temperature T = 300K. A frequency dependent current I = 1nA of bandwidth $\Delta f = 1000Hz$ flows through the junction. Find the ratio between the thermal and shot noise currents $I_{thermal}/I_{shot}$.

Enter the answer here:

(2 points for correct answer)

¹⁸ p18v3TFY4190v2021

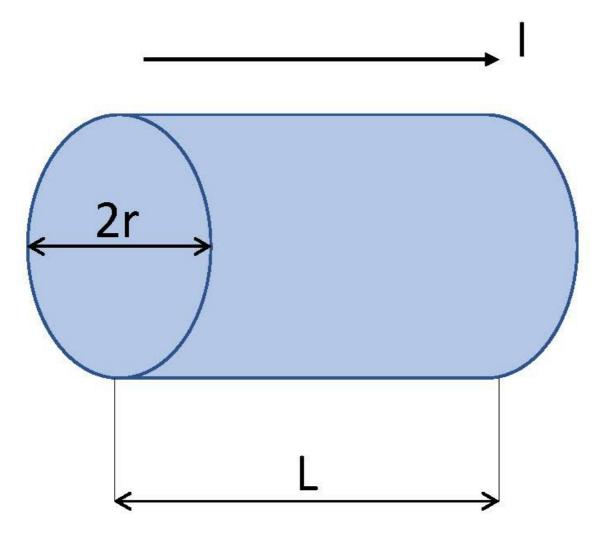

A current flows through a resistor shaped as a cylinder of resistivity ρ , length **L** and radius **r**, as shown in the figure above.

Use Gauss' law of error propagation to estimate the uncertainty in the dissipated power in the resistor when the relative uncertainties in dimensions are given by $\frac{\Delta r}{r} = 0.02$ and $\frac{\Delta L}{L} = 0.01$. The relative uncertainty in the current measurement is $\frac{\Delta I}{I} = 0.005$.

Enter the answer in % here:

(2 points for correct answer)

Solution Exam June 10, 2021

Problem 1

-213 -> -11010101 -> (add one digit) -011010101 -> 100101011 (2comp)

Problem 2

$$\frac{I_1}{I_x} = 4 \text{ and } \frac{V_0}{R} = -(I_1 + I_2 + I_3) = -V_i \left(\frac{1}{2R} + \frac{1}{4R} + \frac{1}{8R}\right) = -\frac{7V_i}{8R} \Rightarrow V_0 = -\frac{7}{8}V_i = -4.375V_i$$

Problem 3

Sign -, exponent 1000 0100 = 128+4 -bias 127 = 5, fraction = 0.25+0.125+0.0625 = 0.4375

Number = $-2^5 \times 1.4375 = 46.00$

Problem 4

<x> = 5.070, Precision = 100(1-(5.2-5.060)/5.060) = 97.23%

Problem 5

RMS average =
$$\sqrt{\frac{1}{T}\int_0^T \sin^2\omega t dt} = \sqrt{\frac{\omega}{2\pi}\int_0^{\frac{2\pi}{\omega}} \sin^2\omega t dt} = \sqrt{\frac{1}{2\pi}\int_0^{2\pi} \sin^2x dx} = \sqrt{\frac{1}{2}} = 0.707$$

Rectified average = $\frac{2}{T}\int_0^{\frac{T}{2}} \sin\omega t dt = \frac{\omega}{\pi}\frac{1}{\omega}[-\cos x]_0^{\pi} = \frac{2}{\pi} = 0.637$

Problem 6

The voltage decreases when moving away from the load (negative imaginary part of load impedance)

$$V(d) = Be^{j\beta d} \left(1 + \Gamma_{\!R} e^{-j2\beta d} \right) = Be^{j\beta d} \left(1 + |\Gamma_{\!R}| e^{j(-|\varphi| - 2\beta d)} \right)$$

 $\cos(-|\varphi| - 2\beta d)$ decreases as d increases

$$VSWR = \left|\frac{V_{max}}{V_{min}}\right| = \frac{1 - |\Gamma_R|}{1 + |\Gamma_R|} \Longrightarrow |\Gamma_R| = \frac{VSWR - 1}{VSWR + 1} = 0.6$$

Problem 7

$$I = \frac{V - V_N}{\frac{1}{j\omega C_S}} = \frac{V_N (1 + j\omega RC)}{R} \Longrightarrow \frac{V_N}{V} \approx \frac{j\omega RC_S}{1 + j\omega RC} \Longrightarrow \left| \frac{V_N}{V} \right|^2 = \frac{(\omega RC_S)^2}{1 + \omega^2 R^2 C^2}$$
$$C_S = \left| \frac{V_N}{V} \right| \frac{1}{R} \sqrt{\frac{1}{\omega^2} + R^2 C^2} = 1.04 pF$$

Problem 8

 $Resolution = \frac{15 - (-15)V}{2^{16} - 1} = 0.0004578 V$

 $Hex \ 9DE3 = 1001 \ 1101 \ 1110 \ 0011 \ -> \ - \ 110001000011101 = \ - \ 2^{14} + 2^{13} + 2^9 + 2^4 + 2^3 + 2^2 + 2^0 = \ -25117$

Input voltage = -25117 x 0.0004578 V = -11.499 V

Problem 9

Convert 4038.356 to hexadecimal.

4038/16 = 252 + 6/16	0.356*16 = 0.696 + 5
252/16 = 15 + 12/16	0.696*16 = 0.136 +11
15/16 = 0 + 15/15	0.136*16 = 0.176 + 2
	0.176*16 = 0.816 + 2
=> FC6	0.816*16 = 0.056 + 13
	=> 5,11,2,2,13, = 5B22D

Problem 10

Nyquist f_s = 48kHz, f_{cut-off} = 18kHz

Problem 11

$$R(s) = 1 \text{ and } F(s) = \frac{s}{(s+1)(s+2)}$$

From Laplace table $y(t) = f(t) = 2e^{-2t} - e^{-t} = y(0.5s) = 0.13 = 13\%$

Problem 12

$$\Gamma_R = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1+j}{4+j} = \frac{(1+j)(4-j)}{(4+j)(4-j)} = \frac{5}{17} + j\frac{3}{17}$$
$$|\Gamma_R| = \frac{\sqrt{25+9}}{17} = 0.343 \text{ and } \ \angle\Gamma_R = \tan^{-1}\frac{3}{5} = 30.96^\circ$$

Problem 13

$$G(s) = \frac{1}{0.01s^3 + s + 1} \xrightarrow{s = j\omega} G(\omega) = \frac{1}{1 + j(\omega - 0.01\omega^3)} = \frac{1 + j(0.01\omega^3 - \omega)}{1 + (\omega - 0.01\omega^3)^2}$$

$$\angle G(\omega) = \tan^{-1}(0.01\omega^3 - \omega) \text{ since } \tan(180^\circ) = 0, \text{ we get } \omega(180^\circ) = 10 \text{ rad/s}$$

$$\omega T_0 = 2\pi \Rightarrow T_0 = \frac{2\pi}{\omega} = 0.628 \, s$$

Problem 14

$$\left(\frac{\Delta V}{\Delta t}\right)_{max} = 5\omega = 10\pi f = \frac{\Delta V_{resolution}}{4\tau} = \frac{\frac{2 \cdot 5}{2^{14} - 1}}{4\tau}$$
$$\tau = \frac{\frac{1}{2^{14} - 1}}{4\pi \cdot 1000} s = 4.86 \cdot 10^{-9} s = 4.86 ns$$

Problem 15

$$V_G = \frac{V_B}{Z_G + Z_1} Z_1 => V_B = \frac{Z_G + Z_1}{Z_1} V_G = 12V$$

The reflection coefficient must be -1/3.

$$\Gamma_{12} = \frac{Z_2 - Z_1}{Z_2 + Z_1} = -\frac{1}{3} \Longrightarrow 3(Z_2 - Z_1) = -(Z_2 + Z_1) \Longrightarrow Z_2 = 0.5Z_1 = 37.5\Omega$$

The load impedance Z_L must be 0 (shorted).

Problem 16

$$u(t) = \sin(\omega t) = \sin(2\pi f t)$$
$$u_n(t) = \sin(2\pi f n\tau_s) = \sin(2\pi f n\tau_s + m2\pi) = \sin(2\pi [nf + mf_s]\tau_s)$$

There multiples of \mathbf{f} and \mathbf{f}_s may be present in the sampled signal without using a low-pass filter.

Problem 17

$$I_{thermal} = \sqrt{\frac{4k_B T \,\Delta f}{R}} = 1.287 \cdot 10^{-11} \,A = 12.87 \,pA$$
$$I_{shot} = \sqrt{2eI \,\Delta f} = 0.566 \cdot 10^{-13} \,A = 0.566 \,pA \implies \frac{I_{thermal}}{I_{shot}} = 22.75$$

Problem 18

$$P = RI^{2} = \frac{\rho L}{\pi r^{2}}I^{2}$$

$$\frac{dP}{P} = \frac{dL}{L} - 2\frac{dr}{r} + 2\frac{dI}{I}$$

$$Gauss \Rightarrow \frac{\Delta P}{P} = \sqrt{\left(\frac{\Delta L}{L}\right)^{2} + \left(2\frac{\Delta r}{r}\right)^{2} + \left(2\frac{\Delta I}{I}\right)^{2}} = \sqrt{0.01^{2} + 4 \cdot 0.02^{2} + 4 \cdot 0.005^{2}} = 0.042 = 4.2\%$$