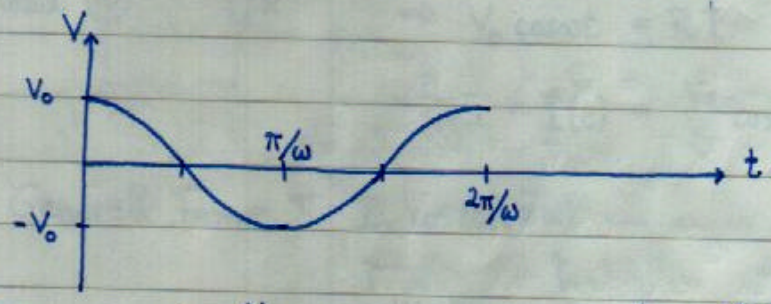


Vekselstrømkretser, impedans

(LHL 27)

Vekselspenning: $V(t) = V_0 \cos \omega t$

Kretssymbol: \sim




Harmonisk svingning

Frekvens: $f = \frac{\omega}{2\pi}$


Periode: $T = \frac{1}{f} = \frac{2\pi}{\omega}$

Amplitude: V_0

Hvordan lage vekselspenning?

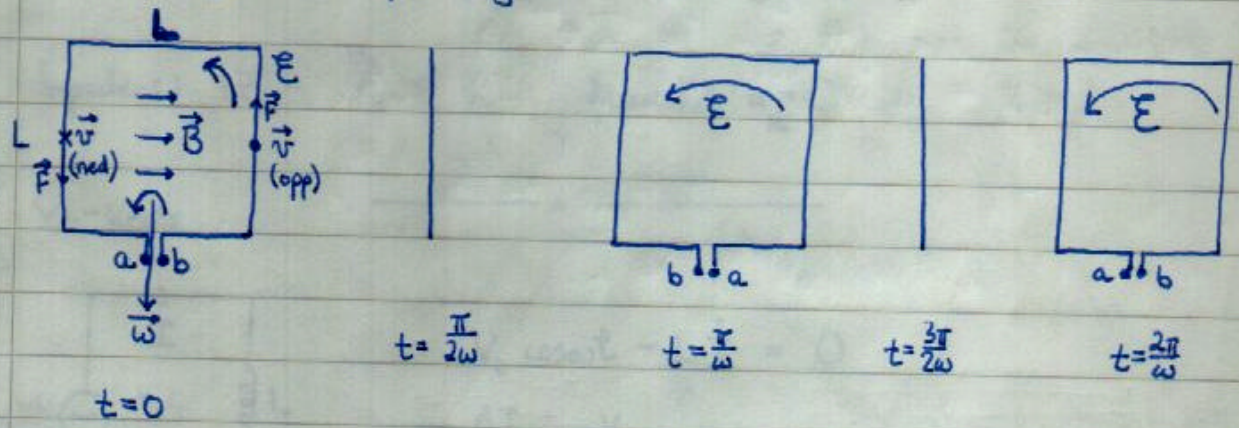

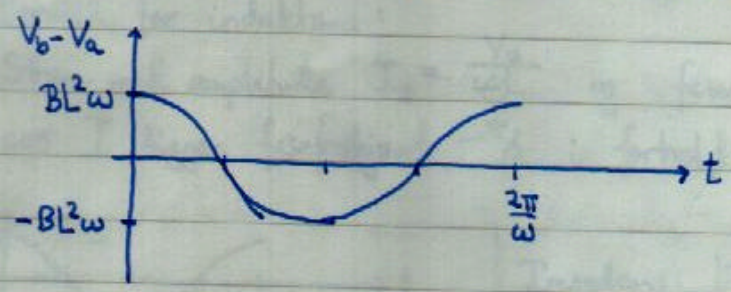
$$\begin{aligned} \mathcal{E} &= - \frac{d\Phi_m}{dt} = -BL^2 \frac{d}{dt} (\cos(\omega t + \pi/2)) = BL^2 \omega \sin(\omega t + \pi/2) \\ &= BL^2 \omega \cos \omega t = V_b - V_a = V_0 \cos \omega t \end{aligned}$$



(NPTT) Impedans : "generaliseret modstand"

VR-krets

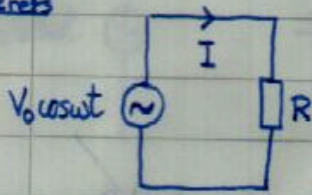

Ohms lov + Kirchhoff

→ V_0 cos wt = RI

⇒ I = I(t) = V_0/R cos wt

Generell form: I = I_0 cos(ωt - α)

↑
amplitude

↑
fasevinkel, dvs: hvor langt "I" ligger i forhold til V?


Modstand: I_0 = V_0/R, α_R = 0, dvs I og V "i fase"

Impedans: |Z| = V_0/I_0 = R; fasevinkel α_R = 0

Helt 14.11.02

kerfra 20.11.02

VL-krets

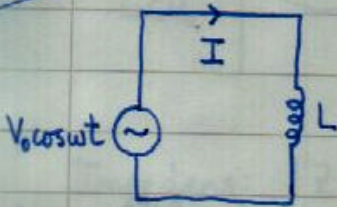


V_0 cos wt - LI = 0

⇒ dI/dt = V_0/L cos wt


⇒ I = V_0/ωL sin wt = V_0/ωL cos(ωt - π/2)

Derved, for induktans:

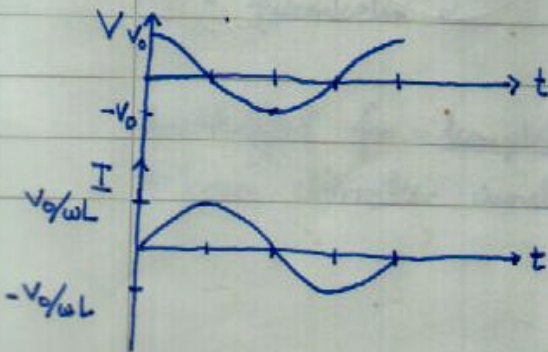Strøm med amplitude I_0 = V_0/ωL og fasevinkel α_L = π/2, dvs I ligger faseforskydet -π/2 i forhold til V



Impedans: |Z| = V_0/I_0 = ωL; fasevinkel α_L = π/2

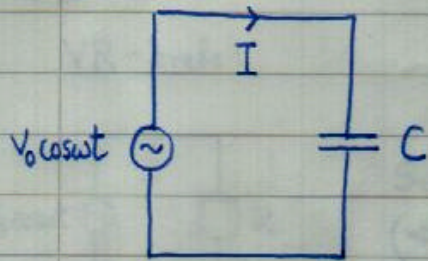

$$V_0 \cos \omega t = Q/C, \quad I = \frac{dQ}{dt}$$



$$\Rightarrow Q = V_0 C \cos \omega t$$

$$I = -V_0 \omega C \sin \omega t$$

$$= V_0 \omega C \cos(\omega t + \pi/2)$$

Dermed, for kapasitans:
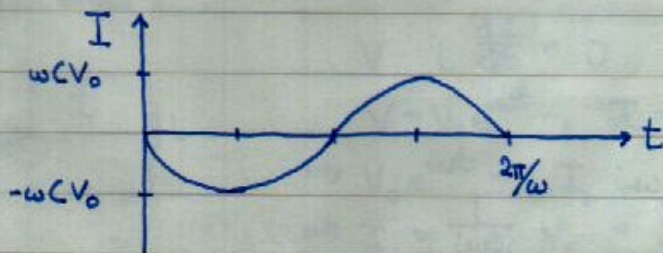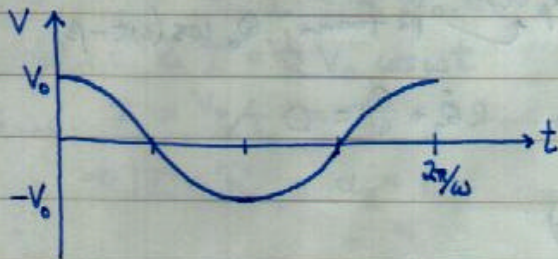
$$I_0 = \omega C V_0, \quad \alpha_c = -\pi/2, \quad \text{dvs } I \text{ ligger } \pi/2 \text{ foran } V$$



$$\text{Impedans: } |Z| = \frac{V_0}{I_0} = \frac{1}{\omega C}; \quad \text{fasevinkel } \alpha_c = -\pi/2$$


Atsæ to interessante størrelser:

- $|Z| = V_0/I_0$ ("hvor stor strøm-amplitude I_0 for gitt V_0 ! ")
- fasevinkelen α ("hvor langt eller ligger I i forhold til V ! ")

Ser på sydd for kompleks notasjon: $Z = |Z| e^{i\alpha}$

→ begge størrelser inneholdt i den komplekse impedansen Z !

VR-krets:

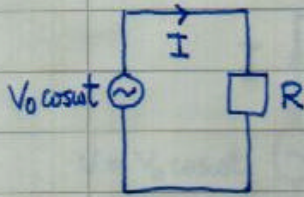

$$V - RI = 0$$

Setter $V = V_0 e^{i\omega t}$, $I = I_0 e^{i\omega t}$
 (\Rightarrow fysisk ems = $\text{Re} V = V_0 \cos \omega t$)

Dermed:

$$V_0 e^{i\omega t} - RI_0 e^{i\omega t} = 0$$

$$\Rightarrow I_0 = \frac{1}{R} V_0$$


$$\Rightarrow I = \frac{1}{R} V_0 e^{i\omega t}$$

Fysisk strøm: $\text{Re} I = \frac{1}{R} V_0 \cos \omega t$ (ok!)

Impedans: $Z = V_0 / I_0 = R$

$$\Rightarrow |Z| = R, \alpha_R = 0 \quad (\text{ok!})$$

VL-krets:

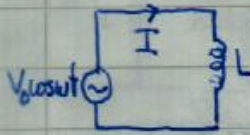

$$V - L \frac{dI}{dt} = 0$$

$V = V_0 e^{i\omega t}$, $I = I_0 e^{i\omega t}$

$$\Rightarrow V_0 e^{i\omega t} - LI_0 i\omega e^{i\omega t} = 0$$

$$\Rightarrow I_0 = \frac{1}{i\omega L} V_0 = \frac{V_0}{\omega L} e^{-i\pi/2}$$

(kompleks; inneholder fasevinkel α_L)


$$\Rightarrow I = \frac{V_0}{\omega L} e^{-i\pi/2} e^{i\omega t}$$

Fysisk strøm: $\text{Re} I = \frac{V_0}{\omega L} \cos(\omega t - \pi/2)$ (ok!)

Impedans: $Z = V_0 / I_0 = i\omega L = \omega L e^{i\pi/2}$

$$\Rightarrow |Z| = \omega L, \alpha_L = \pi/2 \quad (\text{ok!})$$

VC-krets:

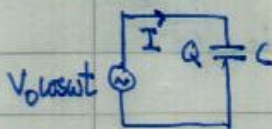

$$V = \frac{Q}{C} \Rightarrow V_0 e^{i\omega t} = \frac{1}{C} Q_0 e^{i\omega t}$$

$$\Rightarrow I = I_0 e^{i\omega t} = \dot{Q} = V_0 C i\omega e^{i\omega t} = \omega C V_0 e^{i\pi/2} e^{i\omega t}$$

Fysisk strøm: $\text{Re} I = \omega C V_0 \cos(\omega t + \pi/2)$ (ok!)


Impedans: $Z = V_0 / I_0 = \frac{1}{i\omega C} = \frac{1}{\omega C} e^{-i\pi/2}$

$$\Rightarrow |Z| = \frac{1}{\omega C}, \alpha_C = -\pi/2 \quad (\text{ok!})$$

4.2.04

RCL-krets, drevne elektriske svingninger

(A&F 27.10)

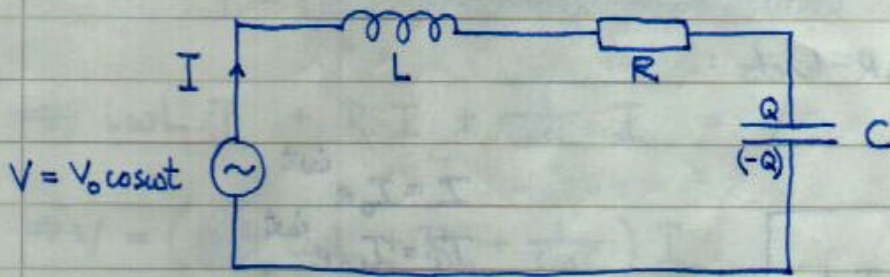


Kirchhoff: $V - LI = RI + \frac{Q}{C}$

$I = \dot{Q}$

$\Rightarrow L\ddot{Q} + R\dot{Q} + \frac{1}{C}Q = V_0 \cos \omega t$

Mekanisk analogi:

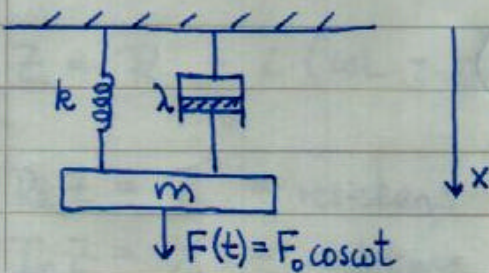

Newton: $F = ma = m\ddot{x}$
 $\Rightarrow F_0 \cos \omega t - \lambda \dot{x} - kx = m\ddot{x}$
 $\Rightarrow m\ddot{x} + \lambda \dot{x} + kx = F_0 \cos \omega t$

\Rightarrow analogt RCL-krets med

- $m \leftrightarrow L$ (tregthed)
- $\lambda \leftrightarrow R$ (motstand)
- $k \leftrightarrow \frac{1}{C}$
- $x \leftrightarrow Q$
- $F_0 \leftrightarrow V_0$ (drivende kraft)

Løsning

Ser på stationær løsning, dvs ikke evt. "innsvingningsforløp"

\Rightarrow kan sette $Q = Q_0 e^{i\omega t}$ og $I = I_0 e^{i\omega t}$ når $V = V_0 e^{i\omega t}$

Dermed: $I = \dot{Q} = i\omega Q$, $Q = \frac{1}{i\omega} I$

$\dot{I} = i\omega I$

$\Rightarrow i\omega L I + R I + \frac{1}{i\omega C} I = V$

$\Rightarrow V = (i\omega L + R + \frac{1}{i\omega C}) I$

$= (Z_L + Z_R + Z_C) I$

$= Z I$


(Seriekobling av ^{komplekse} impedanser: $Z = \sum_i Z_i$ } dvs som for motstandar
 Parallellkobling: $Z^{-1} = \sum_i Z_i^{-1}$ } i likestrømleretsar)

Hitt 20-11-02

$Z = R + i(\omega L - \frac{1}{\omega C}) \equiv R + iX$

$Re Z = R =$ resistans

$Im Z = X =$ reaktans

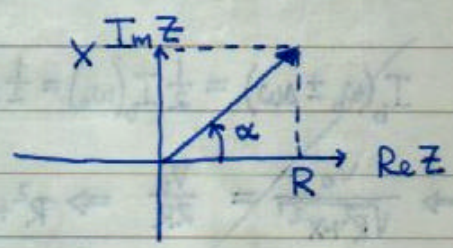

$Z = |Z| e^{i\alpha}$

$\Rightarrow |Z| = \sqrt{(Re Z)^2 + (Im Z)^2} = \sqrt{R^2 + X^2} = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

$\tan \alpha = \frac{X}{R} = \frac{\omega L - \frac{1}{\omega C}}{R}$, $\alpha = \arctan(\frac{X}{R})$

Strømmen:

$I = \frac{V}{Z} = \frac{V_0}{R + iX} e^{i\omega t} = \frac{V_0}{\sqrt{R^2 + X^2}} e^{-i\alpha} e^{i\omega t}$

" fysisk strøm = $Re I = \frac{V_0}{\sqrt{R^2 + X^2}} \cos(\omega t - \alpha)$

" $|I_0| = \frac{V_0}{|Z|} = \frac{V_0}{\sqrt{R^2 + X^2}}$, $\alpha = \arctan(\frac{X}{R})$

KOMMIT 2011

Effekttap i AC-kretser

Tilført energi pr tidsenhet ved tidspunkt t : $P(t) = V(t)I(t)$

$$V(t) = V_0 \cos \omega t, \quad I(t) = I_0 \cos(\omega t - \alpha)$$

$$\Rightarrow P(t) = V_0 I_0 \cos \omega t \cos(\omega t - \alpha)$$

Midlere effekt over en periode $T = \frac{1}{f} = \frac{2\pi}{\omega}$:


$$\langle P \rangle = \frac{1}{T} \int_0^T P(t) dt$$

$$\cos a \cos b = \frac{1}{2} (\cos(a+b) + \cos(a-b))$$

$$= \frac{\omega}{2\pi} \int_0^{2\pi/\omega} V_0 I_0 \frac{1}{2} (\cos(2\omega t - \alpha) + \cos \alpha) dt = \frac{\omega}{2\pi} V_0 I_0 \frac{1}{2} \cos \alpha \frac{2\pi}{\omega}$$

Null bidrag: enkel harmonisk funksjon integrert over 2 hele perioder

$$= \frac{1}{2} V_0 I_0 \cos \alpha$$

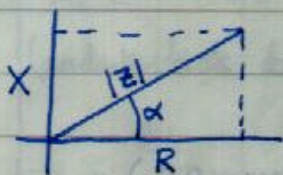


$$\cos \alpha = \frac{R}{|Z|} = \frac{RI_0}{V_0}$$

$$\Rightarrow \langle P \rangle = \frac{1}{2} R I_0^2 = R I_{\text{eff}}^2$$

effektivverdier: $I_{\text{eff}} = \frac{1}{\sqrt{2}} I_0$
 $V_{\text{eff}} = \frac{1}{\sqrt{2}} V_0$

Resonans: $I_0 = \frac{V_0}{\sqrt{R^2 + X^2}}$ maksimal nær $X=0$

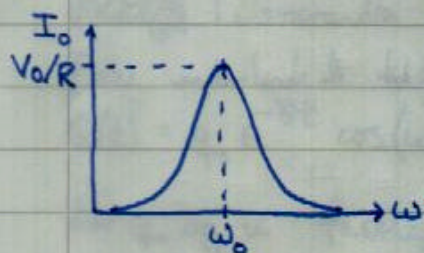For RCL-kretsen: $X(\omega) = \omega L - \frac{1}{\omega C} = 0$ for $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$



Ved resonans:

$$\alpha(\omega = \omega_0) = 0 \Rightarrow I(t) \text{ i fase med } V(t)$$


$$V_L + V_C = 0, \quad V = RI$$

$$Z = R, \quad \langle P \rangle = \frac{1}{2} \frac{V_0^2}{R} \text{ (maksimal)}$$

$\omega_0 =$ kretsens resonansfrekvens

KOM HIT 21.11.

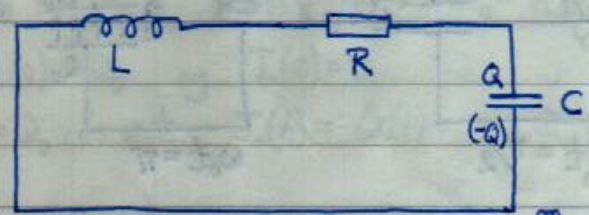
RCL-krets, fri elektriske svingninger (A&F 27.9)



Startbetingelser (t=0): I(0) = I_0, ~~Q(0) = Q_0~~ Q(0) = Q_0

Kirchhoff:

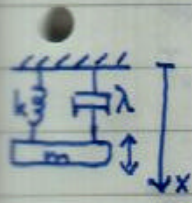-L\dot{I} = RI + \frac{Q}{C}, I = \dot{Q}
\Rightarrow L\ddot{Q} + R\dot{Q} + \frac{1}{C}Q = 0 (evt: L\ddot{I} + R\dot{I} + \frac{1}{C}I = 0)



Mekanisk analogi (m \leftrightarrow L, \lambda \leftrightarrow R, k \leftrightarrow \frac{1}{C}, \epsilon x \leftrightarrow Q) har løsning

x(t) = \begin{cases} x_0 e^{-\gamma t} \cos(\omega t + \alpha) & \gamma = \frac{\lambda}{2m}, \omega = \sqrt{\omega_0^2 - \gamma^2}, \omega_0 = \sqrt{\frac{k}{m}} \\ & \text{(underkritisk damping, } \frac{\lambda}{2m} < \omega_0) \end{cases}

x_1 e^{-\gamma_1 t} + x_2 e^{-\gamma_2 t} & \gamma_{1,2} = -\gamma \pm \sqrt{\gamma^2 - \omega_0^2}

(overkritisk damping, \gamma > \omega_0)

(x_1 + x_2 t) e^{-\gamma t}

(kritisk damping, \gamma = \omega_0)

Startbetingelser, x(0) og \dot{x}(0) fastligger integrationskonstantene x_0, \alpha (evt. x_1, x_2)

~~Udtryk~~ Tilsvarende løsning for Q(t) i RCL-kretsen!

F.eks. underkritisk tilfælde:

Q(t) = q_0 e^{-\gamma t} \cos(\omega t + \alpha) \quad \gamma = \frac{R}{2L}, \omega = \sqrt{\omega_0^2 - \gamma^2}, \omega_0 = \frac{1}{\sqrt{LC}}

der q_0 og \alpha fastlægges ved at Q(0) = Q_0 og I(0) = \dot{Q}(0) = I_0

Energi forhold:

LC-krets: $R=0, \gamma=0 \Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{LC}}$

Anta $Q(0) = Q_0$ og $I(0) = 0$


$\Rightarrow Q(t) = Q_0 \cos \omega_0 t, I(t) = \dot{Q}(t) = -\omega_0 Q_0 \sin \omega_0 t = -I_0 \sin \omega_0 t$

Energi:

$U_C = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C} =$ elektriske energi, "potensiell energi" ($\hat{=} \frac{1}{2} kx^2$)

$U_L = \frac{1}{2} LI^2 = \frac{1}{2} L\dot{Q}^2 =$ magnetisk energi, "kinetisk energi" ($\hat{=} \frac{1}{2} m\dot{x}^2$)

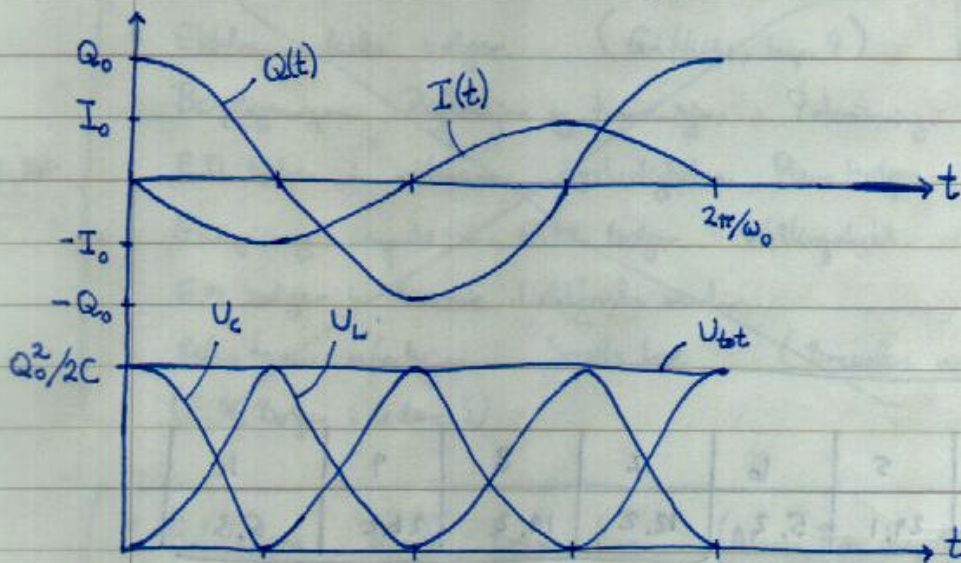$\Rightarrow U_{tot} = U_C + U_L = \frac{1}{2} \frac{Q_0^2}{C} \cos^2 \omega_0 t + \frac{1}{2} L \omega_0^2 Q_0^2 \sin^2 \omega_0 t = \frac{Q_0^2}{2C}$



RCL-krets:

$U_{tot} = U_C + U_L + U_R = \frac{Q^2}{2C} + \frac{1}{2} LI^2 + \int_0^t P(t) dt ; P(t) = \underbrace{RI(t) \cdot I(t)}_{V_R(t)}$

$t \rightarrow \infty : Q, I \rightarrow 0 \Rightarrow U_{tot} = U_R = \int_0^{\infty} RI(t)^2 dt = U(0) = \frac{Q_0^2}{2C}$

