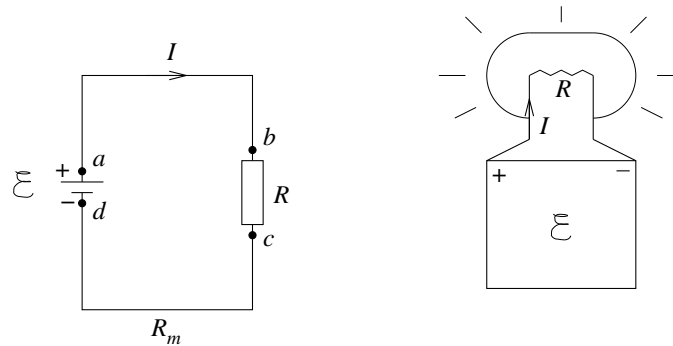


Summary, week 13 (March 30)

DC circuits

[FGT 27; YF 26; TM 25; AF 24.7; LHL 22]


Eksempel: lommelykt



Voltage source (e.g., chemical battery, solar cell etc.):

”Delivers *electromotive force* (emf), i.e., makes sure that we always have a constant potential difference \mathcal{E} between the two ”poles” + and -.

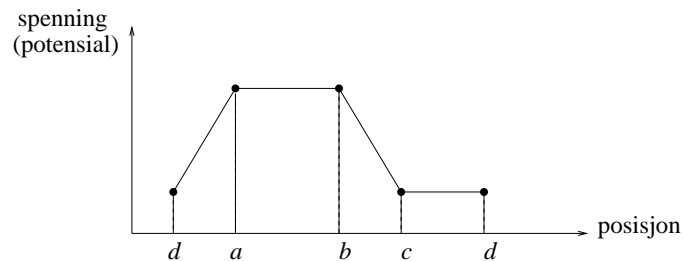Voltage around the circuit in the figure above (ΔV is change in electric potential):




$a \rightarrow b$: $\Delta V \simeq 0$ (metal wire, good conductor, $R_m \simeq 0$, $\mathbf{E} \simeq 0$)

$b \rightarrow c$: $\Delta V = -RI$ (resistor, bad conductor, $R \gg R_m$, potential energy is lost as heat because of collisions, $\mathbf{E} \neq 0$)

$c \rightarrow d$: $\Delta V \simeq 0$ (as $a \rightarrow b$)

$d \rightarrow a$: $\Delta V = \mathcal{E} = RI$ (receives charge carriers with low potential energy, *delivers* charge carriers with high potential energy.)

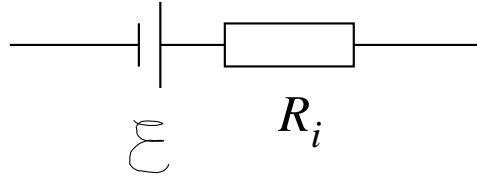A *real* source always has a (usually small) inner resistance R_i :



When a real voltage source is connected to an electric circuit, the inner resistance R_i comes in addition to the circuit resistance R . We then have a power loss both in the source ($P_i = R_i I^2$) and in the rest of the circuit ($P_R = R I^2$).

An *ideal* source has $R_i = 0$.

Kirchhoff's rules

[FGT 27.2, 27.3; YF 26.2; TM 25.5; AF 24.8; LHL 22.3]

Calculations on electric circuits are done with the help of Kirchhoff's rules.

Rule 1 (Current rule): Because of *charge conservation*,

$$\sum_j I_j = 0$$

in all junctions in a circuit.

If not, we would obtain charge accumulation in the junction.

Sign convention: *Positive* I when it goes *out of* the junction.


Rule 2 (Voltage rule): Because of *energy conservation*,

$$\sum(\text{voltage changes}) = 0$$

for all closed loops in a circuit.

If not, we would not have a uniquely determined potential energy for the charge carriers at a given place in the circuit.

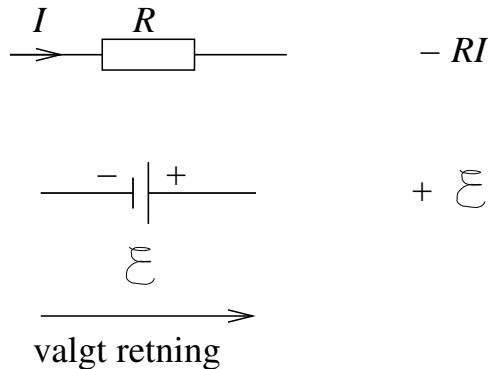Sign convention: *Positive* contribution means *voltage increase*.




Kirchhoff's rules yields a sufficient number of independent equations to determine the unknown quantities, e.g., the currents I_j in the various branches of the circuit.

RC circuits

[FGT 27.5; YF 26.4; TM 25.6; AF Note 25.1; LHL 22.4]

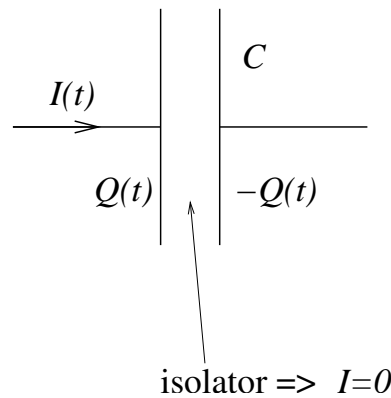The space between the two conductors in a capacitor is filled with an *insulator*, and through an (ideal) insulator runs *zero* electric current.




However, we may have a *time dependent* current $I(t)$ into and out of the conductors of the capacitor (*the plates*, if we have a parallel plate capacitor).

Hence, we obtain a time dependent charge $Q(t)$ on the capacitor plates.

Are we allowed to use Kirchhoff's rules to analyze circuits with time dependent $I(t), V(t), Q(t)$?
 Yes: For "slowly" varying currents, where slow means in comparison to how fast a change at one place in the circuit is "detected" in the rest of the circuit. Since electromagnetic signals (waves) propagate with the speed of light, c , this is in practice usually no problem.

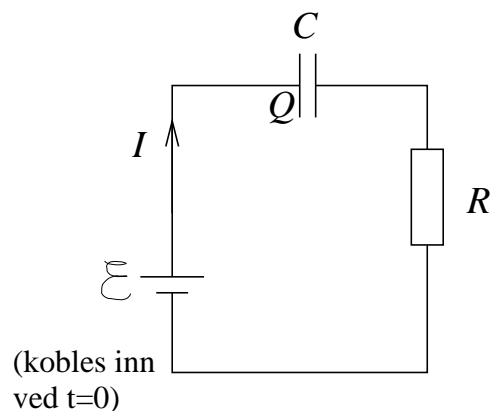Example 1: Charging of capacitor in RC circuit.



The voltage source \mathcal{E} is connected at time $t = 0$. At that instant, we have zero charge on the capacitor, $Q(0) = 0$.

Kirchhoff's voltage rule \Rightarrow

$$\mathcal{E} - V_C - V_R = 0$$

Voltage drop across C :

$$V_C = Q/C$$

Voltage drop across R :

$$V_R = RI = R \frac{dQ}{dt}$$

Yields 1. order differential equation for the charge Q :

$$R \frac{dQ}{dt} + \frac{1}{C}Q = \mathcal{E}$$

which has solution

$$Q(t) = \mathcal{E}C \left(1 - e^{-t/RC}\right)$$

Here, we have used the *initial condition* $Q(0) = 0$.

The current is


$$I(t) = \frac{dQ}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

Time constant for the charging process: $\tau = RC$

The value of τ provides a *time scale* for how long time it takes to charge the capacitor to its maximum charge

$$Q(t \rightarrow \infty) = \mathcal{E}C$$

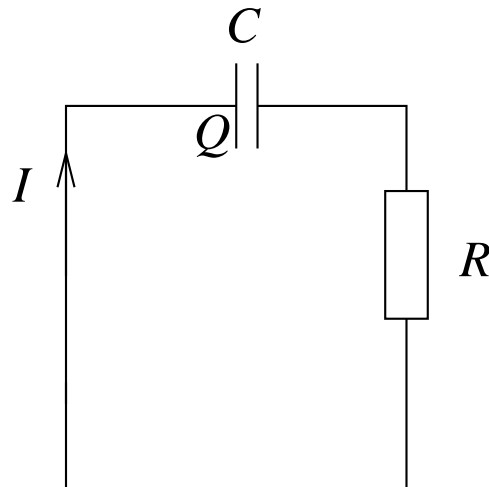Example 2: Discharge of capacitor in RC circuit.



We assume that the capacitor has been charged with a voltage source \mathcal{E} , and that it is fully charged. Hence, the initial condition now is $Q(t = 0) = \mathcal{E}C$.

Kirchhoff's voltage rule \Rightarrow

$$-V_R - V_C = 0$$

Gives, as above, 1. order differential equation for the charge Q :

$$-R\frac{dQ}{dt} - \frac{1}{C}Q = 0$$

which has solution

$$Q(t) = \mathcal{E}C e^{-t/RC}$$

Here, we have used $Q(0) = \mathcal{E}C$.

The current is

$$I(t) = \frac{dQ}{dt} = -\frac{\mathcal{E}}{R}e^{-t/RC}$$

We see from the figure that we chose the "wrong" direction for the current I : Positive charge will flow from the positively charged plate, and therefore give a positive current counterclockwise. However, this is taken into account since the calculated current came out with a negative sign.

Note that is we had chosen the opposite direction for I in the figure, we could no longer write $I = dQ/dt$, but rather $I = -dQ/dt$, since a positive current in that case would correspond to a *reduction* in the charge on the capacitor. In other words: dQ/dt will then be negative for positive I , and we must write $I = -dQ/dt$ to have the same sign on both sides of the equation.

I recommend to choose the direction of I into the plate with charge Q , as done above. Then we may stick to the relation $I = dQ/dt$, i.e., positive I corresponds to a positive change in the charge Q . The initial condition for each particular problem will make sure that the sign of I is correct in the end!

Next week:

Magnetic interactions! We start (in the "ekstratimen" on Tuesday) by showing, or at least indicating, that the magnetic field and magnetic forces are a direct consequence of electrostatics (i.e., that charges at rest influence each other with Coulomb forces) *and* Einstein's special theory of relativity. In other words, we may conclude that *magnetism is a relativistic effect*.

Next, we will consider the movement of a charged particle in a magnetic field, and we will also introduce the *Biot-Savart law*, which gives us the recipe for calculating the magnetic field \mathbf{B} when we know the electric current(s) in our system. The Biot-Savart law is to magnetostatics what Coulomb's law is to electrostatics, how to calculate the electric field \mathbf{E} when we know the electric charges in our system. And, if we know the fields \mathbf{E} and \mathbf{B} , we may proceed to evaluate the force on a given charge q with velocity \mathbf{v} :

$$\mathbf{F} = q\mathbf{E} + q\mathbf{v} \times \mathbf{B}$$

which is the famous *Lorentz force*.