

5

Oppgave 3.


a) Vinkelfrekvensen er $\omega = 2\pi f = 2\pi \cdot 3400\text{s}^{-1} = \underline{2,14 \cdot 10^4 \text{s}^{-1}}$

Med dette finner en:

Motstanden: $Z = R = \underline{80\Omega}$ $\alpha = 0$

Induktansen: $Z = \omega L = 2,14 \cdot 10^4 \cdot 0,45 \cdot 10^{-3} \Omega = \underline{9,6\Omega}$ $\alpha = \frac{\pi}{2} = 90^\circ$

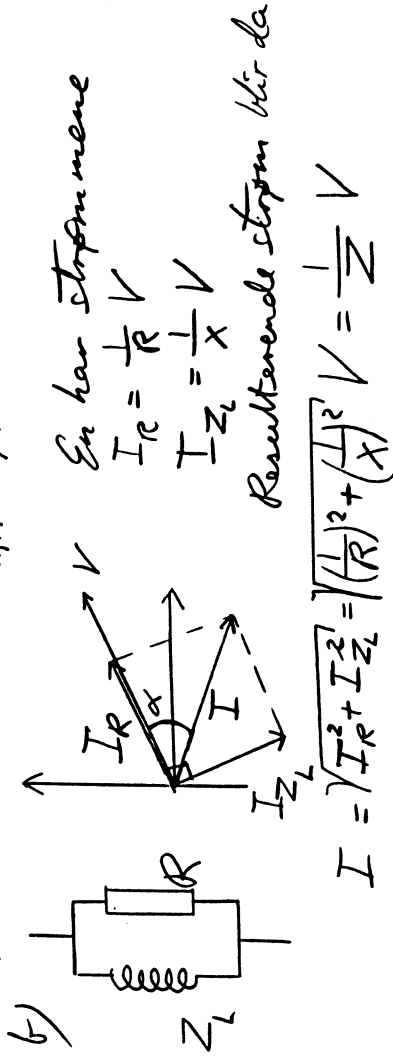Kapasitansen: $Z = \frac{1}{\omega C} = \frac{1}{2,14 \cdot 10^4 \cdot 0,24 \cdot 10^{-9}} = \underline{1,95 \cdot 10^2 \Omega}$ $\alpha = -\frac{\pi}{2} = -90^\circ$



Impedansen blir følgende

$$Z = \left(\frac{1}{R^2} + \frac{1}{X^2} \right)^{-1} \cdot R \cdot X = \frac{30 \cdot 40 \Omega}{\sqrt{30^2 + 40^2}} = \underline{24\Omega}$$

Fasevinkel: $\alpha = \frac{I_{Z_L}}{I_R} = \frac{1/X}{1/R} = \frac{R}{X} = \frac{3}{4} = 0,75$

$$\alpha = \underline{36,9^\circ}$$

Alternativt med komplekse tall:

Parallellkopling: $\frac{1}{Z} = \frac{1}{R} + \frac{1}{Z_L} \Rightarrow Z = \frac{R Z_L}{R + Z_L} =$

$\frac{R \cdot iX}{R + iX} = \frac{RX}{X - iR} = |Z| e^{i\alpha}$, der $|Z| = \frac{RX}{(R^2 + X^2)^{1/2}}$, og $\alpha = \frac{R}{X}$.